 


POWERING DIGITAL BOARDS DISTRIBUTION AND PERFORMANCE

Istvan Novak, Signal Integrity Staff Engineer
SUN Microsystems, Inc.

Meeting of the Greater Boston Chapter
IPC Designer's Council
February 9, 1999



Proliferation of Supply Voltages



In CMOS devices, at every edge, power is dissipated

The power can be lowered by:

- lower capacitance
(smaller feature size)
- lower voltage


$$E = \frac{1}{2} CV^2 \quad P = fCV^2$$

  With submicron feature sizes, the breakdown voltage is below 5 V.
Supply voltages in different circuits (core, IO, memory, etc) drop differently.



Istvan Novak
istvan.novak@
worldnet.att.net

Power Distribution Requirements

 


Larry Smith, "Power Distribution for High Performance Systems,"
Conference Class 4, EPEP98, West Point, NY, October 26-28, 1998

Powering digital boards - distribution and performance 3


IPC Boston Chapter

Feb. 1999

 

Istvan Novak
istvan.novak@worldnet.att.net

Power-Distribution Hierarchy

 


Istvan Novak, Anton Hluscu, "Smart Power Distribution," Trenrew Application Note, 1994

Powering digital boards - distribution and performance 4

IPC Boston Chapter


Feb. 1999

 


Istvan Novak
istvan.novak@worldnet.att.net

SMPS Output Impedance


Measured output impedance of a 50W SMPS

 

 Output impedance varies with input and output conditions (V_{in} , I_{load})



DC Resistance

 

Resistance of a homogeneous square conductor:

$$R = \rho l / A \text{ } [\Omega]$$

ρ: resistivity of material [Ωm]

$$R = R_{\text{sheet}} l/w \text{ } [\Omega]$$

R_{sheet} : sheet resistance (@ ρ, t)

l: length of conductor [unit]

w: width of conductor [unit]

t: thickness of conductor [unit]

Example:

2 ounce (2.76mil, 70 μm)
copper on 6" by 9" PCB:

$$\sigma = 5.85 \cdot 10^7 \text{ } [\text{S/m}]$$

$$R_{\text{DC}} = \mathbf{0.00037 \text{ ohms}}$$


(along the 9" side)

Copper sheet resistance:
679/ T_p [$\mu\Omega$]



T_p : sheet thickness [mils]

$$R_{\text{DC}} = \mathbf{370 \text{ microohms}}$$

(along the 9" side)

 


DC Drop on Planes, Connection

  

Simulated DC voltage drop on a pair of 3"x3.6" one ounce copper planes, with single-point feed at the front corner (left graph) and with line feed (right graph). Model: resistive grid with 0.2" grid size, 25A DC current sink at 1.5"x1.5" from upper left corner.

 The floor grids of graphs represent the simulation grid.



Inductors

Inductors in logic circuits are used for


- * decoupling
- * EMI filtering

Inductance may appear as **side effect**:

- * inductance of **lead-frames**
- * inductance of **connector pins**
- * inductance of **ground returns**
- * inductance of **component leads**

There are different selection criteria for

 - * small-signal filtering
- * high-current decoupling




Istvan Novak
*istvan.novak@
worldnet.att.net*

Inductor Parameters

- * Nominal inductance
- * Tolerance of inductance
- * Rated AC and DC current
- * Temperature dependence (TC)
- * Loss factor
- * Packaging, parasitics


Magnetic materials with high μ are nonlinear, unstable.

 For decoupling and EMI filtering applications, **lossy inductors** are preferable.




Inductor Equivalent Circuit

Linearized model:

 


- * ESR: Effective series resistance
- * **L**: **Nominal inductance**
- * C_p: Equivalent parallel capacitance

 Components in the equivalent circuit are **nonlinear**.




Inductor Parasitics, Decoupling


 
Fair-Rite lossy
inductors:
three half turns



single-turn
SMD

 


Impedance magnitude [ohms]

  



Istvan Novak
istvan.novak@worldnet.att.net

TDK 70ACC453215T SMD L

Measured:



 


Specification:

  


DC Bias, Saturation

   
Variation of total impedance with DC bias and frequency of a Fair-Rite bead.



EMI T-Filters

 

Equivalent Circuit

 


Three-node EMI T filters are optimized for 50-ohm operation.

Using EMI T filters in low-Z high-Z bypassing/decoupling may result in peaky response.

Use lossy ferrites instead.

<http://www.tdk.com>

 


Capacitor Parameters

- * Nominal capacitance
- * Tolerance of capacitance
- * Rated DC voltage (polarization)
- * Quality factor, loss
- * Packaging, parasitics


Dielectric materials with high ϵ_r have several drawbacks. The **capacitance is a function** of:

 - * frequency
- * DC and AC voltage
- * temperature (TC)
- * time (long-term stability)




Capacitor Equivalent Circuit

Simple model:

 

Extended model:

 

C: Nominal capacitance


ESR: Effective series resistance

L_S : Effective series inductance (ESL)

R_S : Equivalent series resistance

R_P : Equivalent parallel resistance

 Components in the equivalent circuit may be frequency dependent and/or nonlinear.



Capacitor Parasitics

1: 1nF chip

ESR= 1Ω ESL= 1.6nH

2: 100nF chip



ESR= $10\text{m}\Omega$ ESL=1nH

3: 220nF foil


ESR= $10\text{m}\Omega$ ESL=8nH

4: 10 μF tantalum bead


ESR= 0.2Ω ESL=6nH

  



Capacitor Banks

 

 5 x 1500uF 0.02 ohm 7nH
10 x 10uF 0.035 ohm 1.2nH
25 x 0.22uF 0.1 ohm 0.5nH




OSCON Bulk Capacitors

  

Standard aluminium:
1500uF 1ohm 20nH


OSCON SP Series:
1500uF 10mohm 5nH

 http://134.180.49.67/compo/os-con/index_e.html




AVX Low Inductance Capacitance LICA

Internal construction:

 


View of BGA connections:

 

Interleaved matrix connections

ESL = 100 pH

 AVX Corporation: Low Inductance Capacitors, S-LICC5M396-C brochure, 1996.



Technology Trend in Packaging of RLC Components (ESL)


2-5 nH

0.5-2 nH

0.3-1 nH


50-200 pH

10-50 pH

 

axial


1970s

 

SMD (length)

late 80s


1206 size

 

SMD (width)

early 90s

0603 size

 

SMD (height)

late 90s


0402 size





buried

years

 
Istvan Novak
istvan.novak@worldnet.att.net



Mounted Inductance

 
 


 Tanmoy Roy, Larry Smith, "ESR and ESL of Ceramic Capacitor Applied to Decoupling Applications," Proceedings of 1998 EPEP, West Point, New York, October 26-28, 1998, pp. 213-216.



Location of Device Filter

  - * Bypass loop must be small
- * Ground connection must be short
- * VCC connection should be inductive and/or lossy (thin trace, ferrite bead)



Integrated Capacitors

Available technologies:

- thin FR4-like cores
- ceramic-filled cores
- TaO thin-film structures

HADCO:


EmCap™

Dk: 20-50

thickness: ≥ 4 mil

capacitance: 2.5nF/inch²

<http://www.hadco.com>

 


Dk: 25

thickness: 0.02mil

capacitance: 2.5nF


K.Y. Chen, W.D. Brown, L. Schaper, "Modeling and Simulation of Thin Film Decoupling Capacitors," Proceedings of the EPEP Conference, October 26-28, 1998, West Point, NY, pp/ 205-208.

<http://www.hidec.engr.uark.edu>

 


Istvan Novak
istvan.novak@worldnet.att.net

Inductance of Planes

 

Simulated inductive voltage drop (mV) on a pair of 3"x3.6" copper planes with 1mil separation. Model: Tline grid with 0.2" grid size, 2A/nsec PWL current sink at 1.5"x1.5" from upper left corner.

 The floor grids of graphs represent the simulation grid.




Istvan Novak
istvan.novak@worldnet.att.net

Buried Capacitance TM

Developed and licenced by
Unysis, Zycon.

Multilayer board

 - * $h = 2 \text{ mils}$
 $= 51 \text{ microns}$
- * $\epsilon_r = 4.5 \text{ (FR4)}$
- * Low inductance $\sim \text{pH}$
- * No signal trace between
- * Layer count increases by two



$$C_i = \epsilon_0 \epsilon_r A/d =$$
$$= 78.4 \text{ pF/cm}^2$$


URL=<http://www.automata.com/news/papers/zycon/toc.htm>

R. Evans, M. Tsuk, "Modeling and Measurement of a High-Performance Computer Power Distribution System," IEEE Trans. on Components, Packaging, and Manufacturing Technology - Part B, Vol. 17, No. 4, Nov. 1994, pp. 467-471.

Powering digital boards - distribution and performance 27

IPC Boston Chapter

Feb. 1999

 

Istvan Novak
istvan.novak@worldnet.att.net

Innerlayer Capacitance of Large PCB

Multilayer
backplane


$h = 0.95 \text{ mm}$

$\epsilon_r = 4.7 \text{ (FR4)}$


$$C_i = \epsilon_0 \epsilon_r A/d = 4.3 \text{ pF/cm}^2$$

**Correction with
pad clearances
is needed**

480 x 110 x 1.5 mm FR4 PCB

 

 M. P. Goetz, "Time and Frequency Domain Analysis of Integral Decoupling Capacitors," IEEE Transactions on Components, Packaging, and Manufacturing Technology - Part B: Advanced Packaging, Vol. 19, August 1996, No.3, pp. 518-522.







Plane Resonances

10"x10"x31mil FR4
planes at 100MHz

Transfer impedance
from Node 4,4

Magnitude and imaginary self impedances

    

Reducing Plane Resonances


Resonances can be suppressed by

- * series DC loss (no good)
- * series AC loss
- * parallel AC loss [1]
- * capacitive damping at selected locations [2]
- * dissipative edge termination [3]

[1] J. Bandyopadhyay, P. Chahal, M. Swaminathan, "Importance of damping and resonance in thin-film integrated decoupling capacitance design," Proceedings of the 6th Topical Meeting on the Electrical Performance of Electrical Packaging, October 27-29, 1997, pp. 31-34.


[2] C. B. O'Sullivan, L. D. Smith, D. W. Forehand, "Developing a Decoupling Methodology with SPICE for Multilayer Printed Circuit Boards," proceedings of the 1998 International Symposium on Electromagnetic Compatibility, Aug 1998, Denver, CO.

 [3] I. Novak, "Reducing Simultaneous Switching Noise on Power Planes by Dissipative Edge Termination," EPEP'98, October 25-27, 1998, West Point, NY.



Istvan Novak
*istvan.novak@
worldnet.att.net*

Reducing EMI by DET

 


First-cut Lumped Bypass Methodology


Identify target impedance/bandwidth \gg bypass capacitance & ESR

Identify di/dt load, $V_{\text{noise_max}}$ \gg plane and bypass-cap inductance

 Identify power-supply response \gg bulk capacitance & ESR




 For detailed analysis, use SPICE with plane, package, and silicon models.




Parallel-C: Resonance

Impedance of bypass capacitors [ohms]

 


Correct Frequency Response

 




Target: 5mohm 10kHz-30MHz

 5 x 1500uF 0.02 ohm 7nH
10 x 10uF 0.035 ohm 1.2nH
25 x 0.22uF 0.1 ohm 0.5nH




Correct Time Response

   10A 10nsec PWL square current source
Lumped capacitors with ESR & ESL



Istvan Novak
istvan.novak@worldnet.att.net

Low-ESR, Frequency Response

 


Target: 5mohm 10kHz-30MHz

5 x 1500uF 0.02 ohm 7nH




10 x 10uF **0.01** ohm 1.2nH

25 x 0.22uF **0.01** ohm 0.5nH

 

Low-ESR, Time Response

   10A 10nsec PWL square current source
Lumped capacitors with ESR & ESL



Istvan Novak
istvan.novak@
worldnet.att.net

Summary

- * Target impedance is in the mohm range
- * Plane DC resistance analysis should be multi point
- * Bypass capacitor ESL must be low
- * Low-ESR capacitors may resonate
- * Power planes have specific resonant frequencies
- * Lumped models may be suitable for first-cut PDS design
- * Detailed PDS design must include
 - component parasitics (ESL, ESR)
 - detailed plane model
 - power supply and package/silicon models are optional

